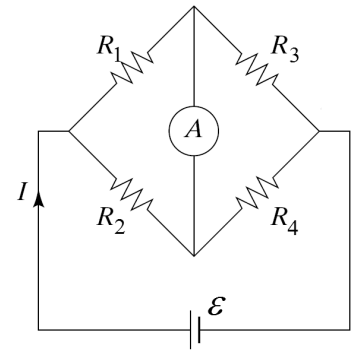


Example


This is a “bridge circuit”. The ammeter A has resistance R_g . The ideal battery has emf \mathcal{E} . What is the relationship among the resistors when the current I_g through the ammeter is zero?



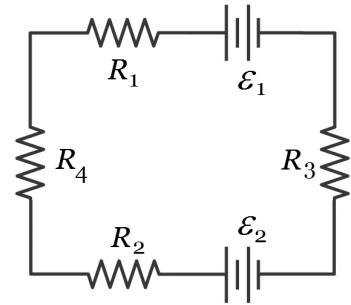Problem


The batteries in the illustrated circuit are *real*. That is, emf \mathcal{E}_1 has internal resistance r_1 , and emf \mathcal{E}_2 has internal resistance r_2 , not shown in the diagram. $\mathcal{E}_2 > \mathcal{E}_1$, so battery 1 is being charged by battery 2.

At what rate magnitude is energy being delivered to battery 1? At what rate magnitude is energy being stored in battery 1?



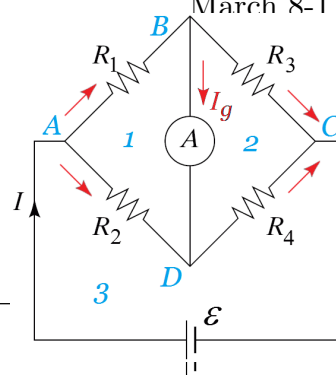Example

This is a "bridge circuit". The ammeter A has resistance R_g . The ideal battery has emf \mathcal{E} . What is the relationship among the resistors when the current I_g through the ammeter is zero?



Choose current directions. Let current I_1 flow through resistor R_1 , etc. Use Kirchoff's node and loop laws. Nodes are lettered A through D . Loops are numbered 1, 2, and 3.

$$A: -I + I_1 + I_2 = 0$$

<1>

$$B: -I_1 + I_g + I_3 = 0$$

<2>

$$D: -I_2 - I_g + I_4 = 0$$

<3>

We chose clockwise as our direction.

we have
loop ①: $I_1 R_1 + I_g R_g - I_2 R_2 = 0$

<4>

loop: ②: $I_3 R_3 - I_4 R_4 - I_g R_g = 0$

<5>

③: $I_2 R_2 + I_4 R_4 = \mathcal{E}$.

<6>

From those 6 equations

Now we ^{only} want to get ($I_g = 0$), so we do not need to solve these six equations together. We put $I_g = 0$ in $\langle 2 \rangle$ & $\langle 3 \rangle$.

$$\Rightarrow I_1 = I_3, \quad I_2 = I_4$$


$$\text{In } \langle 4 \rangle \quad I_1 R_1 = I_2 R_2$$

$$\text{In } \langle 5 \rangle \quad I_3 R_3 = I_4 R_4$$

$$\Rightarrow \frac{R_1}{R_3} = \frac{R_2}{R_4} \Rightarrow R_1 R_4 = R_2 R_3$$

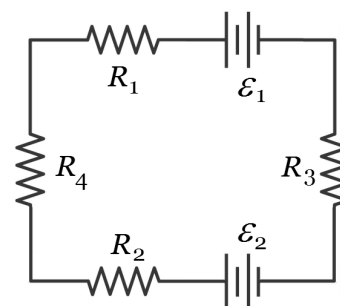Problem

The batteries in the illustrated circuit are *real*. That is, emf \mathcal{E}_1 has internal resistance r_1 , and emf \mathcal{E}_2 has internal resistance r_2 , not shown in the diagram. $\mathcal{E}_2 > \mathcal{E}_1$, so battery 1 is being charged by battery 2.



At what rate magnitude is energy being delivered to battery 1? At what rate magnitude is energy being stored in battery 1?

Remember that power is the rate of energy transfer. Use Kirchoff's Loop Law. Traverse the circuit clockwise, in the known direction of current flow.

$$-I(R_1 + r_1) - I(R_2 + r_2) - I_3 R_3 - I_4 R_4 - \mathcal{E}_1 + \mathcal{E}_2 = 0$$

$$\Rightarrow I = \frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1 + R_2 + R_3 + R_4 + r_1 + r_2}$$

Total power delivered to \mathcal{E}_1 is

$$P = I\mathcal{E}_1 + I^2 r_1$$

$$= \left(\frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1 + R_2 + R_3 + R_4 + r_1 + r_2} \right) \mathcal{E}_1 + \left(\frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1 + R_2 + R_3 + R_4 + r_1 + r_2} \right)^2 r_1$$

The rate that energy is stored in \mathcal{E}_1 is

$$P = I\mathcal{E}_1 = \left(\frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1 + R_2 + R_3 + R_4 + r_1 + r_2} \right) \mathcal{E}_1$$

Note that if magnitudes had not been specified, both of these powers would need to be negative, as power *provided* by a circuit element is considered positive.